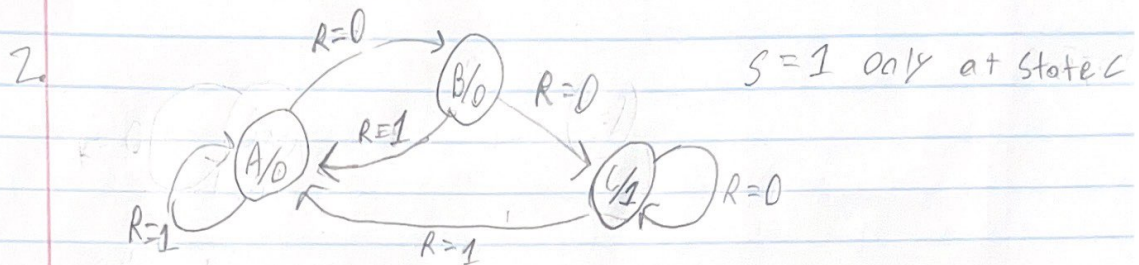


1. You will need 10 bits for the channels because you can get 1024 options which is enough for each state (channel).
You will then need 4 more bits for the volume, has 16 options, enough for 12 levels.



3.


Current state	output
A	1
B	0
C	1

3 states can be represented in 2 bits, so 2 DFFs needed

current	input	next	$Q_1 Q_0$	K	$D_1 D_0$
A	0	B	00	0	01
A	1	A	00	1	00
B	0	C	01	0	10
B	1	C	01	1	10
C	0	A	10	0	00
C	1	B	10	1	01

$$D_0 = \bar{Q}_1 \bar{Q}_0 K + Q_1 \bar{Q}_0 K$$

$$D_1 = \bar{Q}_1 Q_0$$

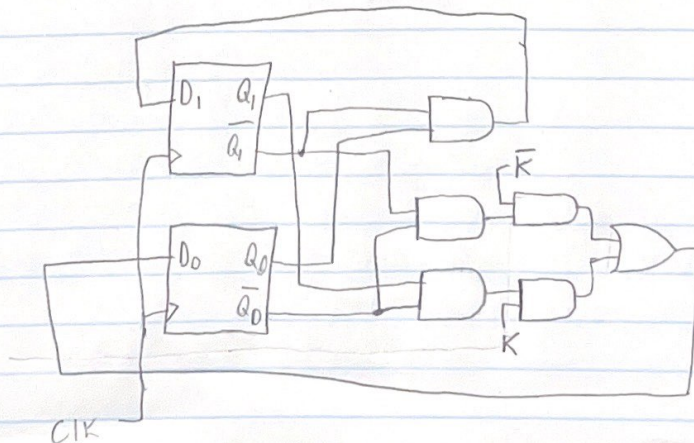

4. Sensor options

L R

0 0

0 1

1 0

1 1

0101 - veers left (turn right)

1010 - veers right (turn left)

0000 - on line (go straight)

States: Going forward, turning right
turning left

